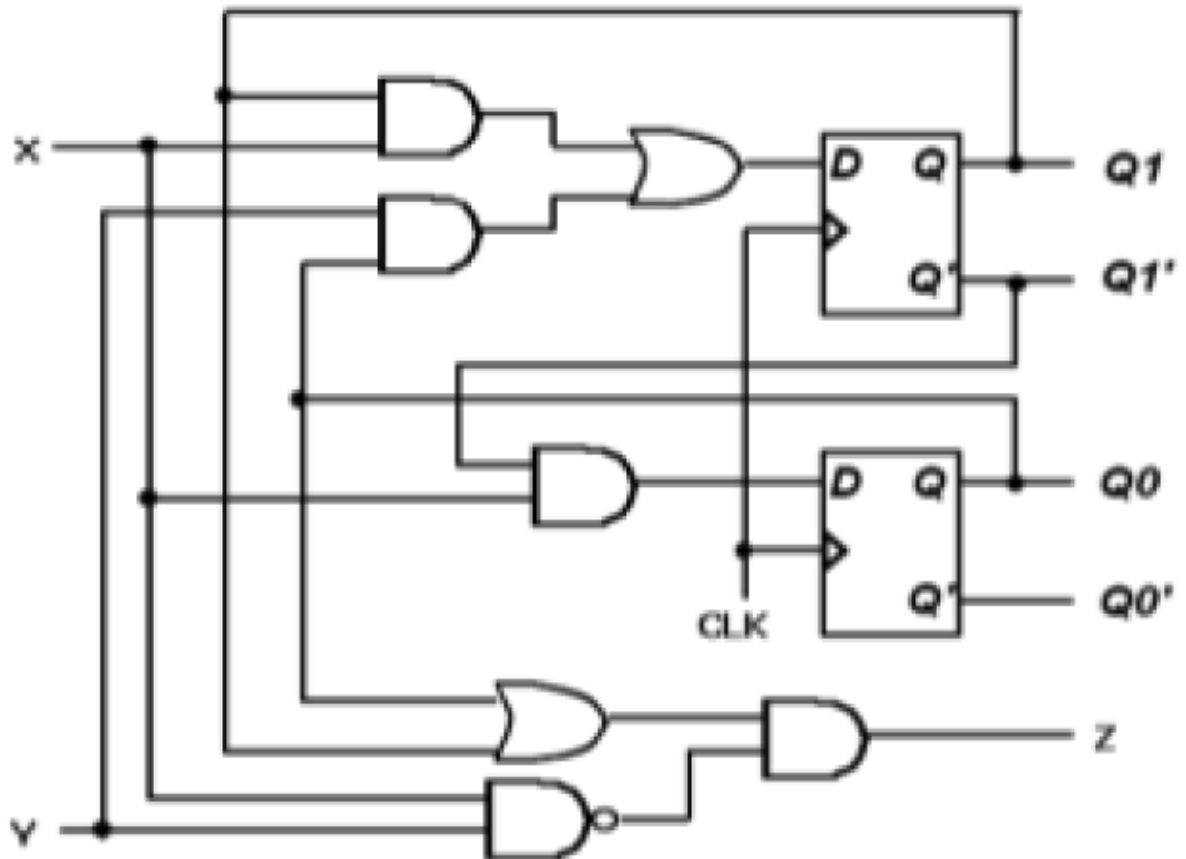


**Assignment 6**  
**COSC 2334**  
**Fall 2021**

Please analyze given state machine and do all steps

1. Determine the excitation equations for the flip-flop control inputs
2. Obtain transition equations by substituting the excitation equations into the flip-flop characteristics equations
3. Construct a transition table by the transition equations
4. Determine the output equations
5. Create a transition/output table by adding output values to the transition for each state (Moore) or state input combinations (Mealy)
6. Obtain a state/output table by naming the states and substitute state names for state-variable combinations in the transition/output table
7. Draw a state diagram corresponding to the state/output table



**Assignment 6**  
**COSC 2334**  
**Fall 2021**

1. Determine the excitation equations for the flip-flop control inputs

$$D0 = (X \& Q1')$$

$$D1 = (Q1 \& X) \text{ OR } (Y \& Q0)$$

2. Obtain transition equations by substituting the excitation equations into the flip-flop characteristics equations

$$Q0^* = D0 = (X \& Q1')$$

$$Q1^* = D1 = (Q1 \& X) \text{ OR } (Y \& Q0)$$

3. Construct a transition table by the transition equations

	<u>XY</u>			
Q0 Q1	00	01	10	11
00	00	00	10	10
01	00	01	01	01
10	00	01	10	11
11	00	01	01	01

4. Determine the output equations

$$Z = ((X \text{ NAND } Y) \& (Q0 \text{ OR } Q1))$$

5. Create a transition/output table by adding output values to the transition for each state (Moore) or state input combinations (Mealy)

	<u>XY</u>				
Q0 Q1	00	01	10	11	Z
00	00	00	10	10	1
01	00	01	01	01	0
10	00	01	10	11	1
11	00	01	01	01	1

6. Obtain a state/output table by naming the states and substitute state names for state-variable combinations in the transition/output table

Q0 Q1	00	01	10	11	Z
A	A	A	C	C	1
B	A	B	B	B	0
C	A	B	C	D	1
D	A	B	B	B	1

7. Draw a state diagram corresponding to the state/output table

Assignment 6  
COSC 2334  
Fall 2021

