

Assignment 3
COSC-2334
Fall 2021

1. (30 points)

• Given: $F = \sum_{w,x,y,z} (0, 1, 2, 3, 4, 5, 7, 14, 15)$

- ▶ Draw a Karnaugh map
- ▶ Find distinguished 1-cells
- ▶ Find the essential prime implicants
- ▶ Draw the reduced map
- ▶ Find the second essential prime implicants
- ▶ Find a minimal sum

Assignment 3
COSC-2334
Fall 2021

2. (20 points)
- a. Explain full subtractor. Design its truth table.
 - b. Express sum and carry based on mean terms and max terms.
 - c. Design its circuit.
 - d. Diagram using basic logic gates (optional).